

Prelab8

Thursday, October 7, 2021 9:06 PM

Your next-state function, reset value and lookup table values

Just as with lab 5, you will implement a unique next-state block, reset value, and output logic for your design. Your next-state table is as follows:

q	next_q
0	1
1	4
2	7
3	6
4	3
5	2
6	5
7	0

Your reset value is 3.

Your first lookup table expression is $X \cdot Y \cdot Z + X \cdot Y \cdot Z' + X \cdot Y' \cdot Z + X' \cdot Y' \cdot Z + X' \cdot Y' \cdot Z'$.

Your second lookup table expression is $X \cdot Y' \cdot Z' + X' \cdot Y \cdot Z + X' \cdot Y' \cdot Z'$.

assign next_q[0] = ~ (p[4] & p[6] & p[2] & p[5])
assign next_q[1] = ~ (p[4] & p[3] & p[5] & p[2])
assign next_q[2] = ~ (p[3] & p[6] & p[2] & p[1])

2 1 0
0 1 1
1 1 0
1 0 1
0 1 0
1 1 1
0 0 0
0 0 1
1 0 0

look at the "1's"

