

- 1) For a function  $F(W,X,Y,Z)$  that has the following truth table, fill in the equivalent Karnaugh map for it, below.

W	X	Y	Z	$F(W,X,Y,Z)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

	W'	W	
Y'			Z'
			Z
Y			Z'
	X'	X	X'

- 2) For the following Karnaugh map, **circle** the essential prime implicants. Draw a **dotted circle** around any non-essential prime implicants.

	W'	W	
Y'	0	1	Z'
	0	1	Z
Y	0	1	Z'
	X'	X	X'

- 3) For the Boolean function  $F(W,X,Y,Z)$  represented by the following Karnaugh map, find a **minimal sum-of-products** expression.

	W'	W	
Y'	1	0	Z'
	1	0	Z
Y	1	1	Z'
	X'	X	X'

$F(W,X,Y,Z) =$  \_\_\_\_\_

- 4) For the Karnaugh map, below, for  $F(W,X,Y,Z)$ , we don't care about some states because their input values are not possible. Create a **minimal sum-of-products** expression for  $F(W,X,Y,Z)$ .

		W'		W		
Y'		1	d	0	1	Z'
		d	1	0	d	
Y		d	1	0	0	Z
		d	d	d	1	Z'
		X'		X		X'

$F(W,X,Y,Z) =$  \_\_\_\_\_


- 6) If the complement of a Boolean function is expressed as a sum of products like this:  $F'(X,Y,Z) = X' \cdot Y \cdot Z + X \cdot Y' \cdot Z$ , then use DeMorgan's law to transform it into a **product of sums** expression for  $F(X,Y,Z)$ .

- 5) For the Karnaugh map, below, for  $F(W,X,Y,Z)$ , we don't care about some states because their input values are not possible. Use the OFF set of the function to create a **minimal sum-of-products** expression for the **complement**,  $F'(W,X,Y,Z)$ .

		W'		W		
Y'		1	d	0	1	Z'
		d	1	0	d	
Y		d	1	0	0	Z
		d	d	d	1	Z'
		X'		X		X'

$F'(W,X,Y,Z) =$  \_\_\_\_\_

 Use the following circuit for questions 7 and 8.



- 7) What kind of hazard exists? (i.e., Static-0 or Static-1?)


- 8) When does the glitch occur?

Use the Karnaugh map, below, for questions 7, 8, and 9. Assume a minimal sum-of-products expression is used to realize the Boolean function  $F(W,X,Y,Z)$  with gates.

		W'		W		
Y'		0	0	1	1	Z'
		0	0	1	1	
Y		0	1	1	1	Z
		0	1	0	0	Z'
		X'	X	X'		

- 9) What kind of logic hazards exist? (i.e., static -1 or static-0)
- 10) Describe W, X, Y, and Z when the glitch occurs.
- 11) Write a complete sum-of-products expression for F that is glitch-free. Do so by adding a single term to the minimal sum-of-product expression.

 - 12) For the Boolean function realized by the circuit, below, complete the truth table. (Reminder: You should not need to evaluate each case if you remember how a network of XOR and XNOR gates can be reduced.)




W	X	Y	Z	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	


Refer to the truth table, below, for questions 13, 14, 15, and 16.

X	Y	Z	F(X,Y,Z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 
- 13) Wire a simple 3-to-8 decoder, with active-high outputs, to a 4-input OR gate to implement the Boolean function.



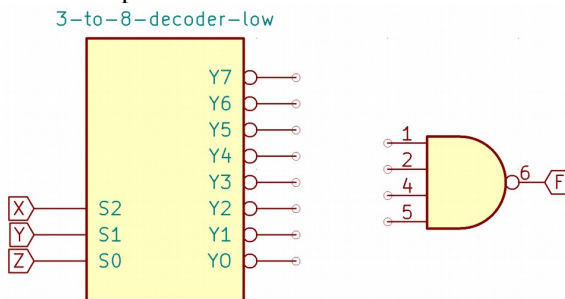
- 14) Wire a 3-to-8 decoder, with active-low outputs, to a 4-input NAND gate to implement the Boolean function.



 
- 15) Wire a 3-to-8 decoder, with active-low outputs, to a 4-input AND gate to implement the Boolean function.



 - 16) Wire the inputs of a simple 8-to-3 multiplexer, with active-high inputs, to either 1 (logic high, or  $V_{DD}$ ) or 0 (Gnd) to implement the Boolean function.



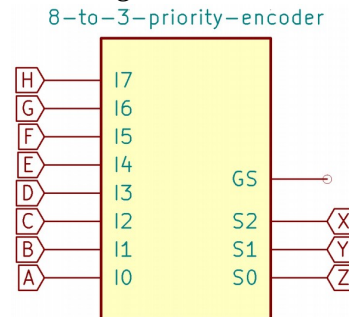- 17) Write a Boolean expression for the Y output of an 8-to-3 priority encoder with active-high inputs and outputs. Express your answer in terms of A, B, C, D, E, F, G, H, or their negations.



Y=\_\_\_\_\_

Here are two example Verilog modules:

```
module xor2(a,b,c);
    input wire a,b;
    output wire [1:0] c;
    assign c = {a,b} ^ 2'b11;
endmodule

module upper(d1,d2,x);
    input wire d1, d2;
    output wire [1:0] x;
    wire [1:0] result;
    xor2 u1(.a(d1), .b(d2), .c(result));
    assign x = ~result;
endmodule
```

- 18) Write a Boolean expression for  $x[0]$  in terms of  $d1$  and  $d2$ .  
Make it as simple as possible.
- 19) Write a Verilog module called 'SoP' that implements the Boolean function  
 $OUT = W \cdot X' \cdot Y \cdot Z + W' \cdot X \cdot Y' \cdot Z' + W \cdot X \cdot Y \cdot Z$   
List the ports in any order.

20) Write a Verilog module named 'invertif' with 1-bit input wires named 'a' and 'doinvert', and a 1-bit output wire named 'out'. 'out' should be the inverse of 'a' if 'doinvert' is high. Otherwise, 'out' should be the value of 'a'.

21) For signals defined in a Verilog module as 'wire [31:0]X;' and 'wire [64:1]Y;', what is the size of the vector, {X[12:3],Y[14:10],X[30:28],X[22:15]}

22) For the following Verilog module,

```
module decode(x,a);
    input wire [2:0]a;
    output wire [7:0]x;
    wire [7:0] map [7:0];
    assign map[0] = 8'h12;
    assign map[1] = 8'h34;
    assign map[3] = 8'h58;
    assign map[6] = 8'hac;
    assign map[7] = 8'hbd;
    assign x = map[a];
endmodule
```


What is the value of x[4] when a == 3'b011 ?

23) For the following Verilog module

```
module priority42(in,s);
  input wire [3:0] in;
  output wire [1:0] s;
  assign s = in[3] == 1 ? 2'b11 :
            in[2] == 1 ? 2'b10 :
            in[1] == 1 ? 2'b01 :
            in[0] == 1 ? 2'b00 :
            2'b00;
endmodule
```

What is the value of s when in == 4'b0110 ?

 24) For the circuit below, write a minimal sum-of-products expression for F(X,Y,Z).



25) For the following Verilog code, what is the value of f when x=1, y=0, z=1?

```
module mux8to1(in,s,out);
  input wire [7:0] in;
  input wire [2:0] s;
  output wire out;
  assign out = (s== 3'b111) ? in[7] :
              (s== 3'b110) ? in[6] :
              (s== 3'b101) ? in[5] :
              (s== 3'b100) ? in[4] :
              (s== 3'b011) ? in[3] :
              (s== 3'b010) ? in[2] :
              (s== 3'b001) ? in[1] :
              in[0];
endmodule

module higher(x,y,z,f);
  input x,y,z;
  output f;
  mux8to1 u1(8'b11001100,{x,y,z},f);
endmodule
```