

- 1) For a function $F(W,X,Y,Z)$ that has the following truth table, fill in the equivalent Karnaugh map for it, below.

W	X	Y	Z	$F(W,X,Y,Z)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

	W'	W	
Y'			Z'
			Z
Y			Z'
	X'	X	X'

- 2) For the following Karnaugh map, draw a **solid circle** around each essential prime implicant for the ON set of the function. Draw a **dotted circle** around each non-essential prime implicant.

	W'	W	
Y'	0	0	Z'
	0	0	Z
Y	1	1	Z'
	0	0	Z
	X'	X	X'

- 3) For the Boolean function $F(W,X,Y,Z)$ represented by the following Karnaugh map, find a **minimal sum-of-products** expression.

	W'	W	
Y'	0	0	Z'
	1	0	Z
Y	1	0	Z'
	0	0	Z
	X'	X	X'


$F(W,X,Y,Z) =$ _____

- 4) For the Karnaugh map, below, for $F(W,X,Y,Z)$, we don't care about some states because their input values are not possible. Create a **minimal sum-of-products** expression for the ON set of $F(W,X,Y,Z)$.

		W'		W		
Y'		0	0	0	d	Z'
		d	0	d	d	
Y		0	d	0	1	Z
		d	1	d	d	Z'
		X'	X	X'		

$F(W,X,Y,Z) =$ _____

 Use the following circuit for questions 6 and 7.



- 6) What kind of hazard exists? (i.e., Static-0 or Static-1?)

- 7) Describe X when the glitch occurs.

- 5) For the Karnaugh map, below, for $F(W,X,Y,Z)$, we don't care about some states because their input values are not possible. Use the OFF set of the function to create a **minimal sum-of-products** expression for the **complement**, $F'(W,X,Y,Z)$.

		W'		W		
Y'		d	0	1	1	Z'
		d	0	d	1	
Y		0	d	d	0	Z
		d	0	d	1	Z'
		X'	X	X'		


$F'(W,X,Y,Z) =$ _____

- 8) The complement of a Boolean function is expressed as a sum of products, $F'(X,Y,Z) = X \cdot Y' \cdot Z + X \cdot Y \cdot Z' + Y \cdot Z$. Use DeMorgan's law to transform it into a **product of sums** expression for $F(X,Y,Z)$.

Use the Karnaugh map, below, for questions 9, 10, and 11. Assume a minimal sum-of-products expression is used to realize the Boolean function $F(W,X,Y,Z)$ with gates.

		W'		W		
Y'		0	0	1	1	Z'
		1	1	1	1	
Y		0	1	0	0	Z
		0	1	0	0	Z'
		X'		X		X'

 12) For the Boolean function realized by the circuit, below, complete the truth table. (Reminder: You should not need to evaluate each case if you remember how a network of XOR and XNOR gates can be reduced.)



9) What kind of logic hazards exist? (i.e., static -1 or static-0)

10) Describe W, X, Y, and Z when the glitch occurs.


11) Write a complete sum-of-products expression for F that is glitch-free. Do so by adding a single term to the minimal sum-of-product expression.

W	X	Y	Z	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	


Refer to the truth table, below, for questions 13, 14, 15, and 16.

X	Y	Z	F(X,Y,Z)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 
- 13) Wire a simple 3-to-8 decoder, with active-high outputs, to a 4-input OR gate to implement the Boolean function.



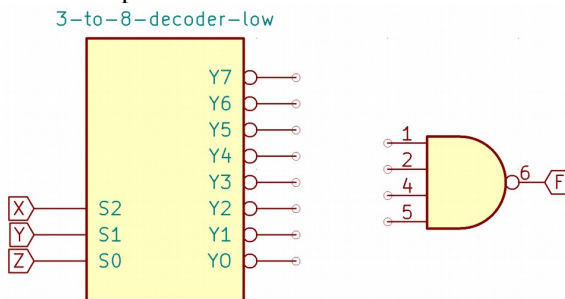
- 14) Wire a 3-to-8 decoder, with active-low outputs, to a 4-input NAND gate to implement the Boolean function.



 
- 15) Wire a 3-to-8 decoder, with active-low outputs, to a 4-input AND gate to implement the Boolean function.



 - 16) Wire the inputs of a simple 8-to-3 multiplexer, with active-high inputs, to either 1 (logic high, or V_{DD}) or 0 (Gnd) to implement the Boolean function.



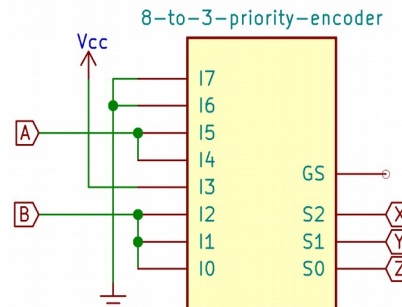- 17) Write a Boolean expression for the X output of an 8-to-3 priority encoder with active-high inputs and outputs. Express your answer in terms of A or B or their negations.



X= _____

Here are two example Verilog modules:

```
module fun(p,q,r,s);
    input wire p,q;
    output wire r,s;
    assign {r,s} = {p & q, p ^ q};
endmodule
```

```
module fun2fa(a,b,x);
    input wire [1:0] a, b;
    output wire [2:0] x;
    wire c1,c2,c3;
    fun u0(.p(a[0]), .q(b[0]),
          .r(c1), .s(x[0]));
    fun u1(.p(a[1]), .q(c1),
          .r(c2), .s(s1));
    fun u2(.p(b[1]), .q(s1),
          .r(c3), .s(x[1]));
    assign x[2] = c2 | c3;
endmodule
```

- 18) Write a Boolean expression for $x[0]$ in terms of $a[1:0]$ and $b[1:0]$. Make it as simple as possible.
- 19) Write a Verilog module called 'SoP' that implements the Boolean function $F = X' \cdot Y \cdot Z + X' \cdot Y' \cdot Z' + X \cdot Y' \cdot Z$. List the ports in any order. Be sure to use proper Verilog syntax for any AND, OR, or NOT operators.

20) Write a Verilog module named 'snooze' with 1-bit input wires named 'a' and 'b', and a 1-bit output wire named 'out'. 'out' should be '1' if and only if 'a' is high, and 'b' is low.

21) For signals defined in a Verilog module as 'wire [68:0]X;' and 'wire [23:1]Y;', state the size of the following vector: {X[8:7],Y[12:11],X[9:6],X[10:2]}

22) For the following Verilog module,

```
module decode(x,a);
    input wire [2:0]a;
    output wire [7:0]x;
    wire [7:0] map [7:0];
    assign map[0] = 8'hf1;
    assign map[1] = 8'he2;
    assign map[2] = 8'hd3;
    assign map[3] = 8'hc4;
    assign map[4] = 8'hb5;
    assign map[5] = 8'ha6;
    assign map[6] = 8'h97;
    assign map[7] = 8'h88;
    assign x = map[a];
endmodule
```


What is the value of x[3:0] when a == 3'b110 ?
Express your answer as a Verilog binary literal.
Yes, we just want the lower 4 bits of x.
In binary. You can do it!

23) For the following Verilog module

```
module priority42(in,s);
  input wire [3:0] in;
  output wire [2:0] s;
  assign s = in[3] == 1 ? 3'b111 :
            in[2] == 1 ? 3'b110 :
            in[1] == 1 ? 3'b101 :
            in[0] == 1 ? 3'b100 :
            3'b000;
endmodule
```

What is the value of s when in == 4'b1010 ?

 24) For the circuit below, write a minimal sum-of-products expression for F(X,Y,Z).



25) For the following Verilog code, what is the value of f when x=1, y=1, z=0?

```
module mux8to1(in,s,out);
  input wire [7:0] in;
  input wire [2:0] s;
  output wire out;
  assign out = (s== 3'b111) ? in[7] :
              (s== 3'b110) ? in[6] :
              (s== 3'b101) ? in[5] :
              (s== 3'b100) ? in[4] :
              (s== 3'b011) ? in[3] :
              (s== 3'b010) ? in[2] :
              (s== 3'b001) ? in[1] :
              in[0];
endmodule

module multi(x,y,z,f);
  input x,y,z;
  output [2:0]f;
  mux8to1 u2(8'b10010101,{x,y,z},f[2]);
  mux8to1 u1(8'b01010011,{x,y,z},f[1]);
  mux8to1 u0(8'b01100101,{x,y,z},f[0]);
endmodule
```