
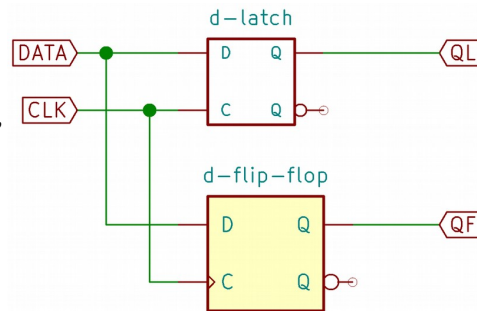



Use the following circuit consisting of a latch and a D flip-flop for the next two questions. Assume that, for each device in question, $t_{pHL}(C \rightarrow Q) = 5 \text{ ns}$, $t_{pLH}(C \rightarrow Q) = 10 \text{ ns}$, $t_{pHL}(D \rightarrow Q) = 15 \text{ ns}$, and $t_{pLH}(D \rightarrow Q) = 20 \text{ ns}$. (Not all parameters are relevant to all devices.) Assume that all setup and hold requirements are met. The initial states of QL and QF are 0.

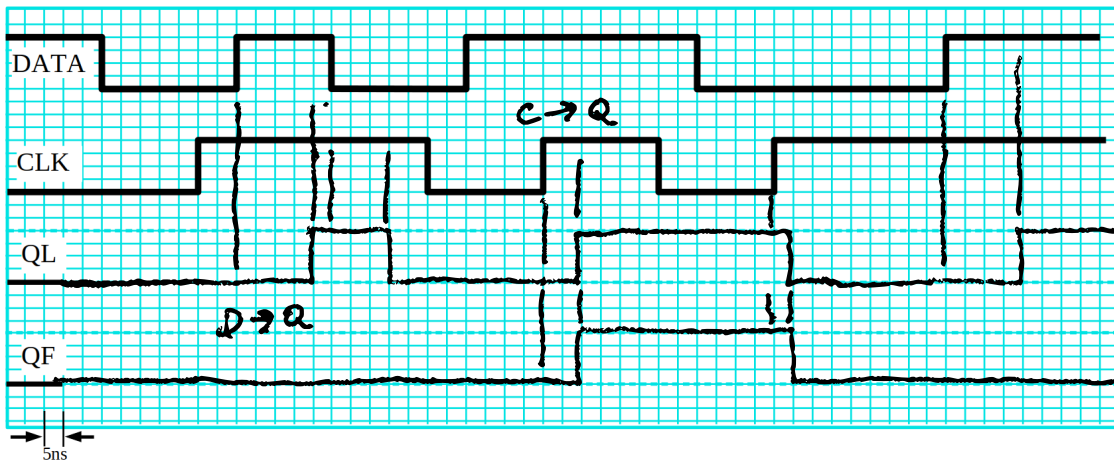

- 1) On the timing diagram below, draw the expected signal for QL.
- 2) On the same diagram below, draw the expected signal for QF.



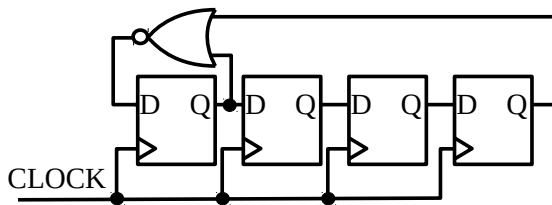
- 3) For the figure below, assume that $t_{pHL}(C \rightarrow Q)$ and $t_{pLH}(C \rightarrow Q)$ for the flip-flops are both 11 ns. The setup time (t_s) for the flip-flops is 7 ns. The hold time (t_h) for the flip-flops is 0 ns. The propagation delays (t_{pHL} and t_{pLH}) for the NOR gate are 5 ns. If CLOCK is a periodic square wave, what is the minimum period that will avoid any flip-flop exhibiting metastability while the circuit still performs as it is expected to?



$$t = 11 + 7 + 5 = 23 \text{ ns}$$

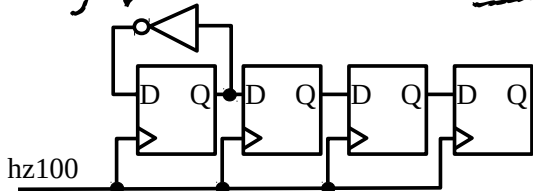- 4) For the figure below, if hz100 is a 100 Hz square wave, describe the out4 signal.

Tricky question – it is not a 4 on 25 Hz signal!



initialized to 0000:

| cycles | pattern |
|--------|---------|
| 1 | 1000 |
| 2 | 0100 |
| 3 | 1010 |
| 4 | 0101 |


$$\begin{array}{r} 5 \overline{) 1010} \\ 6 \overline{) 0101} \end{array}$$

→ out4 = 1 after 4 clock cycles

© 2019 by Purdue University – may not be copied or reproduced, in any form or by any means.

After initial "miss", but after 2 clock cycles
 \therefore 50 Hz goes from 0 → 1 again

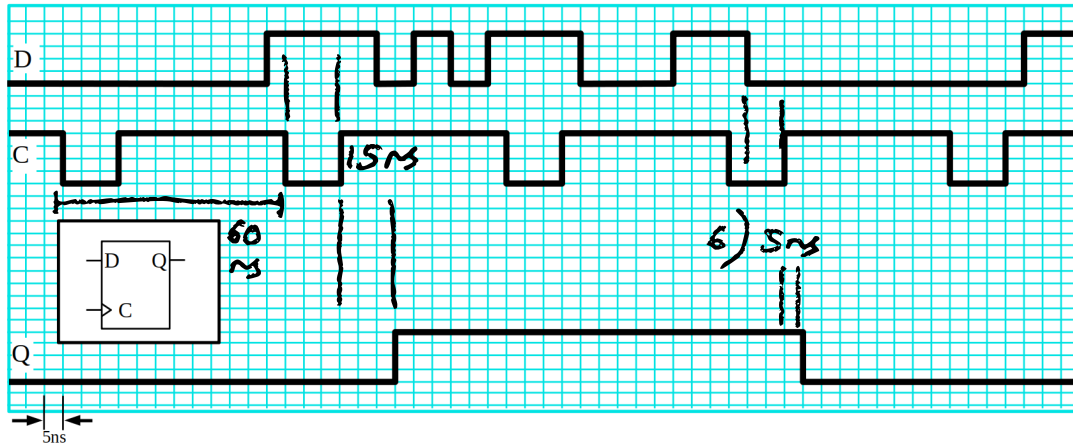Use the diagram below for the following questions about the use of a D flip-flop.



- 5) What type of event causes the flip-flop to copy the D input value to the Q output?

Rising edge of C.

- 6) What is $t_{pHL}(C \rightarrow Q)$? (in nanoseconds, not tickmarks)

5ns

- 7) What is $t_{pLH}(C \rightarrow Q)$? (in nanoseconds)

15ns

- 8) What is the nominal setup time? (in nanoseconds)

10ns

- 9) What is the nominal hold time? (in nanoseconds)

5ns

- 10) What is the clock period? (in nanoseconds)

60ns

- 11) What is the clock's pulse width? (in nanoseconds)

45ns

- 12) What is the clock's duty cycle?

$$45/60 = 75\%$$

- 13) For the following Verilog statements, cross out all **begin** and **end** statements that can be removed without changing the behavior of the design.

```

always @ (posedge clock, posedge reset) begin
  if (reset == 1'b1) begin
    x <= 1'b0;
  end
  else if (a == 1'b1) begin
    x <= y;
  end
  else begin
    x <= 1'b1;
  end
  z <= x;
end

```

Treated as single block

Separate from if/else block.

Technically legal, but could be confusing.

← necessary because there is a statement other than a single if/else block.

- 14) For the following Verilog statements, how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

```

reg x,y;
wire z, clock;
...
always @ (posedge clock) begin
  y = z;
  x = y;
end

```

Flip-flop sensitive to rising edge of clock.

Blocking assignments, so what happens is: $x = y = z$; $\therefore 1 \text{ FF. } (x)$

- 15) For the following Verilog code, how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

```

reg [2:0] x;
wire [1:0] n;
...
always @ (*) begin
  case (n)
    2'b00: x = 3'b101;
    2'b01: x = 3'b000;
    2'b10: x = 3'b111;
    // Note: forgot the case for 2'b11.
  endcase
end

```

always-latch? Five.

always-comb? No, that's an inferred latch error.

Be careful - x is 3-bits long, so there are 3 latches, not 1!

- 16) For the following Verilog statements, how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

```
reg x,y;
wire a,b,c;
...
always @ (*) begin
    if (a == 1) begin
        x = b;
    end
    else begin
        y = c;
    end
end
end
```

Different LHS.
Only assigns on one condition
and not the inverse -
latch! \therefore 2 latches. (x,y)

- 17) For the following Verilog statements, how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

```
reg x;
wire a,b;
...
always @ (*) begin
    if (a == 1)
        x = b;
end
```

Very simple at this point
- 1 latch (x)

- 18) For the following Verilog statements,

```
reg x;
wire a,b;
...
always @ (*) begin
    if (b == 1'b0)
        x = a;
    else
        x = ~a;
end
```


or,

$x = b ? \sim a : a;$


Immediately know this is
combinational, not a
latch.

what kind of circuit will be produced to realize this specification in hardware? (i.e., what is the relationship between x, a, and b?)

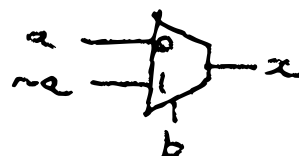Will also accept "a mux with ' $\sim a$ ' and ' a ' as inputs, ' b ' as a select line, and ' x ' as the output."



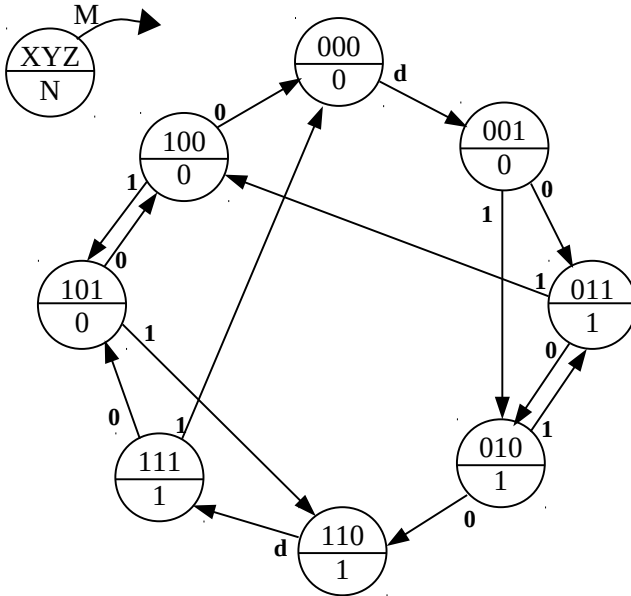19) Given the following state-transition diagram, complete the present state / present output / next state table, and use it for the rest of the questions on this page.



| X | Y | Z | M | N | X* | Y* | Z* |
|---|---|---|---|---|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |

20) The start state is 000. If M is always 0, what repeating output pattern is produced on N?

000 001 011 010 110 111 101 100 000
 0 0 1 1 1 1 0 0 stop

21) The start state is 000. If M is always 1, what repeating output pattern is produced on N?

000 001 010 011 100 101 110 111 000
 0 0 1 1 0 0 1 1 stop

22) For the following Moore machine, whose start state is 000, choose next state values such that the Z bit follows the pattern: **0 1 1 1 1 0 0 0 1 1 1 1 0 0 ...**

Note that there are many arrangements of next state values that will produce the correct pattern for the Z bit, and many others that will not. You do not need to make an optimal choice. Any next state combination that produces the correct pattern for Z is as good as any of the others. Draw a line through any unused states.

| X | Y | Z | X* | Y* | Z* |
|---|---|---|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | | | |
| 1 | 1 | 1 | 0 | 1 | 0 |

000
001
011
101
111
010
100

Do not forget to set this "return state"!

23) For the following Verilog code complete the counter equations to implement a 4-bit synchronous up-counter that resets at strange starting and maximum values.

```

reg [3:0] Q;
assign left[0] = Q[3];
always @ (posedge hz100, posedge reset) begin
    if (reset == 1)          begin Q <= 4'b0111; end
    else if (Q == 4'b1011)   begin Q <= 4'b0111; end
    else                     begin Q <= next_Q; end
end

always @ (Q) begin
    next_Q[0] = ~Q[0];

    next_Q[1] = Q[1] ^ Q[0];

    next_Q[2] = Q[2] ^ &Q[1:0];

    next_Q[3] = Q[3] ^ &Q[2:0];
end

```

24) For the previous question, if the hz100 signal is a 100 Hz square wave, at what frequency does the LED on left[0] flash? (You may express your answer as a fraction.)

$$4'b0111 \rightarrow 4'b1011 = 5 \text{ clock cycles.} \therefore \frac{100 \text{ Hz}}{5 \text{ cycles}} = 20 \text{ Hz}$$

$\hookrightarrow 7 \qquad \qquad \hookrightarrow 11$

- 25) Complete the Verilog case statement below to implement a sequence recognizer that will light the **green** LED if it reads the input sequence 0 0 1 1 on pb[1] at each rising edge of pb[0]. Once **green** is illuminated, it should remain on until reset. If, at any point, the input sequence diverges from 0 0 1 1, it should illuminate **red** and keep it lit until reset.

```

module top(hz100, reset, red, green, ..., pb);
    input hz100, reset;
    output red, green;
    input [20:0] pb;

    reg [2:0] state, next;

    always @ (posedge pb[0], posedge reset) begin
        if (reset == 1'b1) begin
            state <= 3'b000;
        end
        else begin
            state <= next;
        end
    end

    assign green = state == 3'b100; // show green for state 100
    assign red = state == 3'b111; // show red for state 111

    always @ (*) begin
        case ({state, pb[1]})

            default: next = 3'b111; // go to red ←
            4'b0000: next = 3'b001; // advance to 001
            // Complete the implementation below...
            4'b0010: next = 3'b010;
            4'b0101: next = 3'b011;
            4'b0111: next = 3'b100;
            4'b1000: next = 3'b100;
            4'b1001: next = 3'b100;
            // no need to implement
            // case if pb[1] does not
            // match. Why? Already handled.

        endcase
    end
endmodule

```

See pb[1]
pattern:
0 0 1 1
and move to
corresponding
next state:
001, 010,
011, 100
1
sets green = 1'b1