 


The diagram illustrates a circuit with two sequential logic components: a d-latch and a d-flip-flop. Both components share a common DATA input and a common CLK input. The d-latch, represented by a blue box, has inputs D and C, and outputs Q and Q-bar. The d-flip-flop, represented by a yellow box, has inputs D and C, and outputs Q and Q-bar. The DATA input is connected to the D input of both components. The CLK input is connected to the C input of both components. The output of the d-latch (Q) is labeled QL, and the output of the d-flip-flop (Q) is labeled QF.

-
- The timing diagram shows the following signal behavior over a 5ns period:
- DATA:** A square wave that is high from 0 to 1ns, low from 1 to 2ns, high from 2 to 3ns, low from 3 to 4ns, and high from 4 to 5ns.
 - CLK:** A square wave that is low from 0 to 1ns, high from 1 to 3ns, low from 3 to 4ns, high from 4 to 4.5ns, low from 4.5 to 5ns, and high from 5ns to the end.
 - QL:** Remains low (0) throughout the entire duration.
 - QF:** Remains low (0) throughout the entire duration.


- 3) What happens when a D flip-flop becomes metastable?
- 4) Describe three circumstances that could cause metastability with a D flip-flop.

Use the diagram below for the following questions about the use of a D flip-flop.



- 5) What edge of the clock is the flip-flop “triggered” on?
- 6) What is $t_{pHL(C \rightarrow Q)}$? (in nanoseconds)
- 7) What is $t_{pLH(C \rightarrow Q)}$? (in nanoseconds)
- 8) What is the nominal setup time? (in nanoseconds)
- 9) What is the nominal hold time? (in nanoseconds)
- 10) What is the clock period? (in nanoseconds)
- 11) What is the clock’s pulse width? (in nanoseconds)
- 12) What is the clock’s duty cycle?

13) For the figure below,

 

assume that $t_{pHL}(C \rightarrow Q)$ and $t_{pLH}(C \rightarrow Q)$ for the flip-flops are both 10 ns. The setup time (t_s) for the flip-flops is 10 ns. The hold time (t_H) for the flip-flops is 0 ns. The propagation delays (t_{pHL} and t_{pLH}) for each NAND gates is 5 ns. If the clock is a periodic square wave, what is the minimum period that will avoid the second flip-flop exhibiting metastability?

14) For the following Verilog statements,

```
always @ (posedge clock, posedge reset) begin
    if (reset == 1) begin
        x <= 0;
        y <= 0;
    end
    else if (a == 1'b1) begin
        x <= y;
        y <= z;
    end
    else begin
        x <= 1;
    end
end
```

cross out all **begin** and **end** statements that are not necessary.

15) For the following Verilog statements,

```
reg x,y;
wire z;
...
always @ (posedge clock) begin
    x = y;
    y = z;
end
```

how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

16) For the following Verilog statements,

```
reg x;
wire a,b,c;
...
always @ (a,b,c) begin
    if (a == 1) begin
        x = b;
    end
    else begin
        x = c;
    end
end
end
```

how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

17) For the following Verilog statements,

```
reg x;
wire a,b,c;
...
always @ (*) begin
    if (a == 1)
        x = b;
end
```


how many state elements are needed to realize this specification in hardware, and are they flip-flops or latches?

18) For the following Verilog statements,

```
reg x;
wire a,b;
...
always @ (*) begin
    if (b == 0)
        x = 1'b0;
    else
        x = a;
end
```

what kind of circuit will be produced to realize this specification in hardware? (i.e., what is the relationship between **x**, **a**, and **b**?)

 19) Given the following state-transition diagram, complete the present state / present output / next state table, and use it for the rest of the questions on this page.



X	Y	Z	M	N	X*	Y*	Z*
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

20) The start state is 000. If M is always 0, what repeating output pattern is produced on N?

21) The start state is 000. If M is always 1, what repeating output pattern is produced on N?

- 22) For the following Moore machine, whose start state is 000. Choose next state values such that the Z bit follows the pattern: **0 0 0 1 1 0 0 0 0 1 1 0 ...**

Note that there are many arrangements of next state values that will produce the correct pattern for the Z bit, and many others that will not. You do not need to make an optimal choice. Any next state combination that produces the correct pattern for Z is as good as any of the others.

X	Y	Z	X*	Y*	Z*
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

- 23) For the following Verilog code, meant to run on the FPGA development system, complete the counter equations to implement a 4-bit synchronous up-counter.

```

reg [3:0] Q;
assign left[0] = Q[3];
always @ (posedge hz100, posedge reset) begin
    if (reset == 1)          begin Q <= 4'b0000; end
    else if (Q == 4'b1001)   begin Q <= 4'b0000; end
    else                     begin Q <= next_Q;   end
else
    always @ (Q) begin
        next_Q[0] =

        next_Q[1] =

        next_Q[2] =

        next_Q[3] =
    end

```

- 24) For the previous question, at what frequency does the LED on left[0] flash? (You should assume that the hz100 wire is a 100 Hz square wave.)

-
- 25) Complete the Verilog always block body to implement a circular shift register that outputs one element of the repeating sequence 0 0 0 0 1 1 1 on the left[0] output each time it sees the rising edge of pb[0] and resets the sequence to the beginning on the rising edge of pb[1].

```
module top(hz100, left, pb);
    input hz100;
    output [7:0] left;
    input [20:0] pb;

    reg [6:0] shift;

    assign left[0] = shift[6];

    // Write your always block in the space below...
```

```
endmodule
```